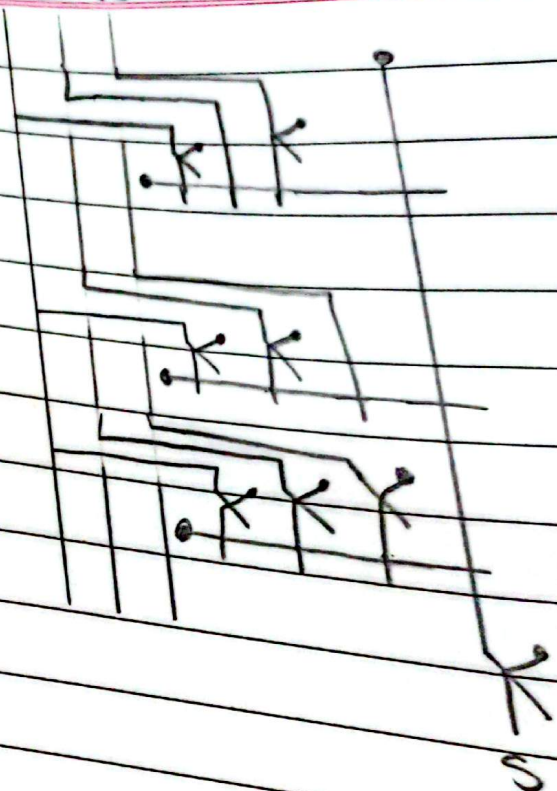


Q.10.

B	D	W	S	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	0	
1	1	0	1	$BD'W$
1	1	1	1	BDW'
			1	BDW

B D W

Boolean: $BD + BW = S$ $S = B(D + W)$